

第 23 章 : 対称3相交流回路

23.2 対称3相交流回路

23.3 対称3相交流電圧のY- Δ 変換

23.5 3相負荷インピーダンスのY- Δ 変換

キーワード : Δ - Δ 結線, Y- Δ 変換, Δ -Y変換

学習目標 : 平衡 Δ - Δ 結線, Y- Δ 変換, Δ -Y変換を理解できる。


23 対称3相交流回路

23.2 対称3相交流回路


(2) Δ - Δ 結線



$$E_{ab} = Z_{ab}I_{ab} \quad (1)$$

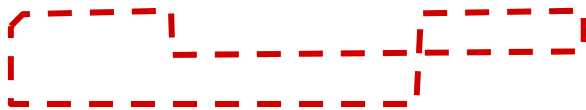

$$E_{bc} = Z_{bc}I_{bc} \quad (2)$$

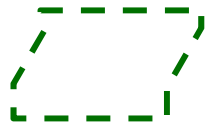


$$E_{ca} = Z_{ca}I_{ca} \quad (3)$$

よって

$$\begin{aligned} E_{ab} + E_{bc} + E_{ca} &= E\angle 0^\circ + E\angle -120^\circ + E\angle -240^\circ \\ &= E + E\left(-\frac{1}{2} - j\frac{\sqrt{3}}{2}\right) + E\left(-\frac{1}{2} + j\frac{\sqrt{3}}{2}\right) = 0 \end{aligned}$$

$$E_{ab} + E_{bc} + E_{ca} = 0$$

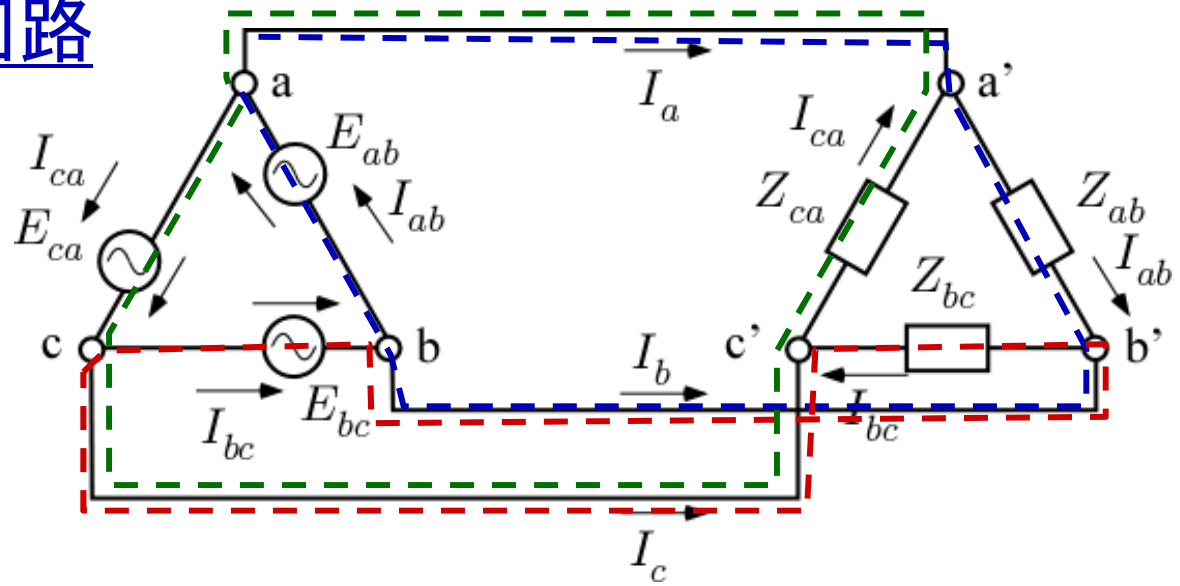

$$I_{ab} = I \angle 0^\circ$$

$$I_{bc} = I \angle -120^\circ$$

$$I_{ca} = I \angle -240^\circ$$

のとき

$$\begin{aligned} I_a &= I_{ab} - I_{ca} \\ &= I \angle 0^\circ - I \angle -240^\circ = I - I \left(-\frac{1}{2} + j\frac{\sqrt{3}}{2} \right) = I \left(\frac{3}{2} - j\frac{\sqrt{3}}{2} \right) \\ &= I \sqrt{\left(\frac{3}{2} \right)^2 + \left(\frac{\sqrt{3}}{2} \right)^2} \angle -30^\circ = I \sqrt{\frac{12}{4}} \angle -30^\circ \\ &= \sqrt{3}I \angle -30^\circ \end{aligned}$$

$$\begin{aligned}
I_b &= I_{bc} - I_{ab} \\
&= I\angle -120^\circ - I\angle 0^\circ = I\left(-\frac{1}{2} - j\frac{\sqrt{3}}{2}\right) - I = I\left(-\frac{3}{2} - j\frac{\sqrt{3}}{2}\right) \\
&= I\sqrt{\left(\frac{3}{2}\right)^2 + \left(\frac{\sqrt{3}}{2}\right)^2} \angle -150^\circ = I\sqrt{\frac{12}{4}} \angle -150^\circ \\
&= \sqrt{3}I \angle -150^\circ
\end{aligned}$$

$$\begin{aligned}
I_c &= I_{ca} - I_{bc} \\
&= I\angle -240^\circ - I\angle -120^\circ = I\left(-\frac{1}{2} + j\frac{\sqrt{3}}{2}\right) - I\left(-\frac{1}{2} - j\frac{\sqrt{3}}{2}\right) \\
&= j\sqrt{3}I \\
&= I\angle -270^\circ
\end{aligned}$$

$$\text{(線電流)} = \text{(相電流)} \times \sqrt{3} \angle -30^\circ$$

(相電流)

$$I_{ab} = I$$

$$I_{bc} = I \angle -\frac{2}{3}\pi = I \angle -120^\circ$$

$$I_{ca} = I \angle -\frac{4}{3}\pi = I \angle -240^\circ$$

(線電流)

$$I_a = \sqrt{3}I \angle -30^\circ$$

$$I_b = \sqrt{3}I \angle -150^\circ$$

$$I_c = \sqrt{3}I \angle -270^\circ$$

$$\text{(相電圧)} = \text{(線電圧)}$$

【問題26.5】

$$I_{ab} = \frac{50\angle 0^\circ}{5} = 10\angle 0^\circ$$

$$I_{bc} = \frac{50\angle -120^\circ}{5} = 10\angle -120^\circ$$

$$I_{ca} = \frac{50\angle -240^\circ}{5} = 10\angle -240^\circ$$

$$I'_{ab} = I_{ab} = 10\angle 0^\circ$$

$$I'_{bc} = I_{bc} = 10\angle -120^\circ$$

$$I'_{ca} = I_{ca} = 10\angle -240^\circ$$

$$I_a = \sqrt{3}I_{ab}\angle -30^\circ = 10\sqrt{3}\angle -30^\circ$$

$$I_b = \sqrt{3}I_{bc}\angle -30^\circ = 10\sqrt{3}\angle -150^\circ$$

$$I_c = \sqrt{3}I_{ca}\angle -30^\circ = 10\sqrt{3}\angle -270^\circ$$

23 対称3相交流回路

23.3 対称3相交流電圧のY-Δ変換



$$E_{ab} = E_a - E_b$$

$$E_{bc} = E_b - E_c$$

$$E_{ca} = E_c - E_a$$

Δ結線の電圧 = $\sqrt{3}$ |Y結線の電圧| $\angle 30^\circ$

大きさは $\sqrt{3}$ 倍, 位相は 30° 進む

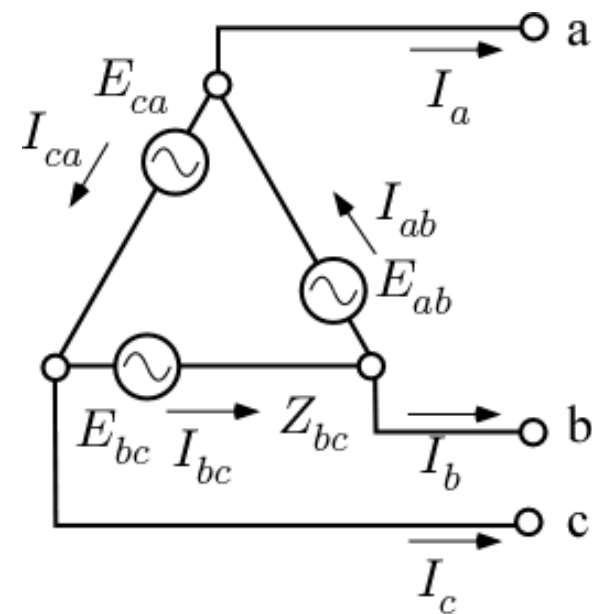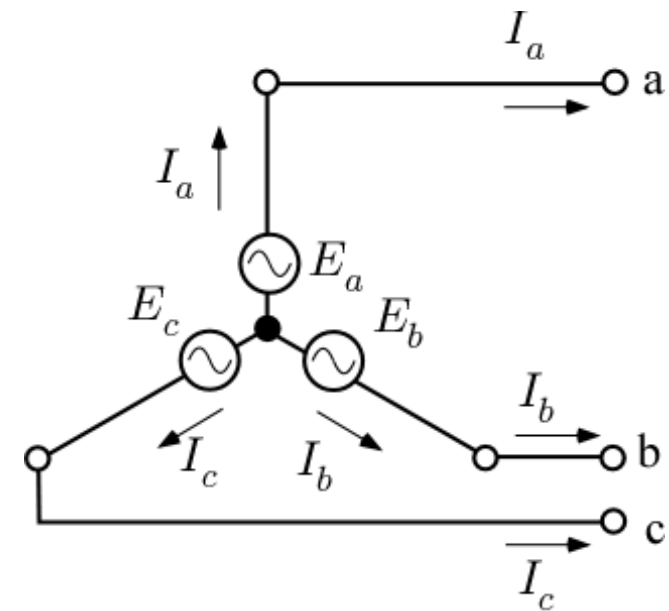

(証明)

$$E_a = E \angle 0^\circ$$

$$E_b = E \angle -120^\circ$$

$$E_c = E \angle -240^\circ$$

のとき

$$E_{ab} = E - E \left(-\frac{1}{2} - j\frac{\sqrt{3}}{2} \right) = E \left(\frac{3}{2} + j\frac{\sqrt{3}}{2} \right) = \sqrt{3}E \angle 30^\circ$$

$$E_{bc} = E \left(-\frac{1}{2} - j\frac{\sqrt{3}}{2} \right) - E \left(-\frac{1}{2} + j\frac{\sqrt{3}}{2} \right) = E \left(-j\sqrt{3} \right) = \sqrt{3}E \angle -90^\circ$$

$$E_{ca} = E \left(-\frac{1}{2} + j\frac{\sqrt{3}}{2} \right) - E = E \left(-\frac{3}{2} + j\frac{\sqrt{3}}{2} \right) = \sqrt{3}E \angle -210^\circ$$

23 対称3相交流回路

23.5 3相負荷インピーダンスのY- Δ 変換

$$Z_a = \frac{Z_{ab}Z_{ca}}{Z_{ab} + Z_{bc} + Z_{ca}}$$



$$Z_b = \frac{Z_{bc}Z_{ab}}{Z_{ab} + Z_{bc} + Z_{ca}}$$

$$Z_c = \frac{Z_{ca}Z_{bc}}{Z_{ab} + Z_{bc} + Z_{ca}}$$

$$Z_{ab} = \frac{Z_aZ_b + Z_bZ_c + Z_cZ_a}{Z_c}$$

$$Z_{bc} = \frac{Z_aZ_b + Z_bZ_c + Z_cZ_a}{Z_a}$$
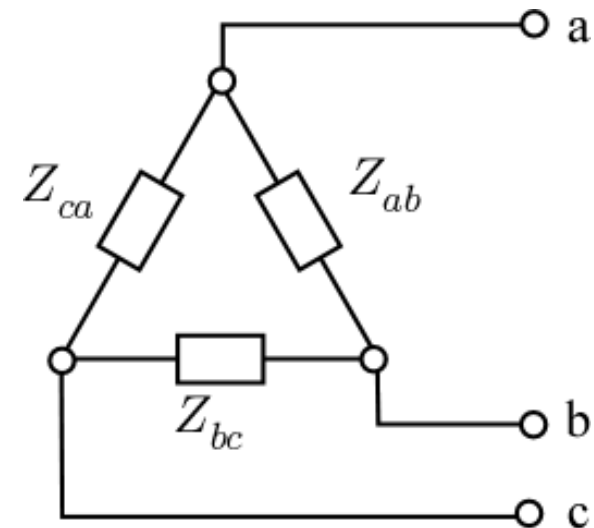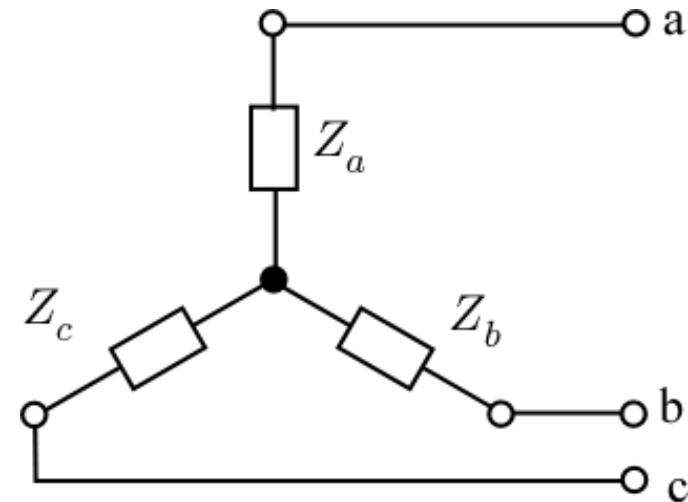
$$Z_{ca} = \frac{Z_aZ_b + Z_bZ_c + Z_cZ_a}{Z_b}$$




$Z_{ab} = Z_{bc} = Z_{ca} = Z$ のとき

$$Z_a = \frac{Z_{ab}Z_{ca}}{Z_{ab} + Z_{bc} + Z_{ca}} = \frac{Z}{3}$$

$$Z_b = \frac{Z_{bc}Z_{ab}}{Z_{ab} + Z_{bc} + Z_{ca}} = \frac{Z}{3}$$
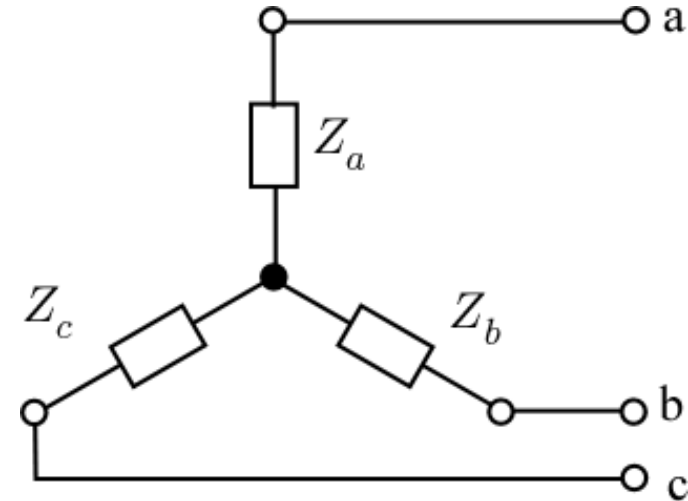
$$Z_c = \frac{Z_{ca}Z_{bc}}{Z_{ab} + Z_{bc} + Z_{ca}} = \frac{Z}{3}$$




$Z_a = Z_b = Z_c = Z$ のとき

$$Z_{ab} = \frac{Z_a Z_b + Z_b Z_c + Z_c Z_a}{Z_c} = 3Z$$

$$Z_{bc} = \frac{Z_a Z_b + Z_b Z_c + Z_c Z_a}{Z_a} = 3Z$$
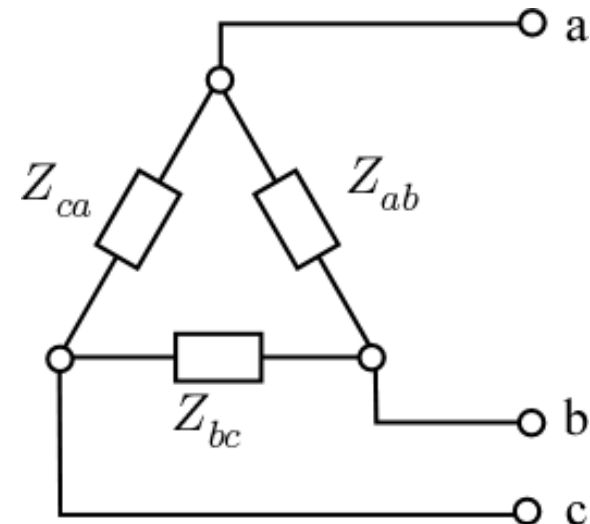
$$Z_{ca} = \frac{Z_a Z_b + Z_b Z_c + Z_c Z_a}{Z_b} = 3Z$$



(証明)

a – b 間のインピーダンス

$$Z_{ab} = Z_a + Z_b = \frac{1}{\frac{1}{Z_{ab}} + \frac{1}{Z_{ca} + Z_{bc}}} = \frac{Z_{ab}(Z_{bc} + Z_{ca})}{Z_{ab} + Z_{bc} + Z_{ca}} \quad (1)$$

b – c 間のインピーダンス

$$Z_{bc} = Z_b + Z_c = \frac{1}{\frac{1}{Z_{bc}} + \frac{1}{Z_{ab} + Z_{ca}}} = \frac{Z_{bc}(Z_{ca} + Z_{ab})}{Z_{ab} + Z_{bc} + Z_{ca}} \quad (2)$$

c – a 間のインピーダンス

$$Z_{ca} = Z_c + Z_a = \frac{1}{\frac{1}{Z_{ca}} + \frac{1}{Z_{ab} + Z_{bc}}} = \frac{Z_{ca}(Z_{ab} + Z_{bc})}{Z_{ab} + Z_{bc} + Z_{ca}} \quad (3)$$

(1) ~ (3) 式を足し合わせる

$$2(Z_a + Z_b + Z_c) = 2 \frac{Z_{ab}Z_{bc} + Z_{bc}Z_{ca} + Z_{ca}Z_{ab}}{Z_{ab} + Z_{bc} + Z_{ca}}$$
$$Z_a + Z_b + Z_c = \frac{Z_{ab}Z_{bc} + Z_{bc}Z_{ca} + Z_{ca}Z_{ab}}{Z_{ab} + Z_{bc} + Z_{ca}} \quad (4)$$

(4) 式 - (2) 式

$$Z_a = \frac{Z_{ab}Z_{ca}}{Z_{ab} + Z_{bc} + Z_{ca}}$$

(4) 式 - (3) 式

$$Z_b = \frac{Z_{bc}Z_{ab}}{Z_{ab} + Z_{bc} + Z_{ca}}$$

(4) 式 - (1) 式

$$Z_c = \frac{Z_{ca}Z_{bc}}{Z_{ab} + Z_{bc} + Z_{ca}}$$

【問題 26.6】

電源をY型に変換

$$V'_a = \frac{60}{\sqrt{3}} \angle -30^\circ = 20\sqrt{3} \angle -30^\circ$$

$$V'_b = \frac{60}{\sqrt{3}} \angle -150^\circ = 20\sqrt{3} \angle -150^\circ$$



$$V'_c = \frac{60}{\sqrt{3}} \angle -270^\circ = 20\sqrt{3} \angle -270^\circ$$

電流

$$I_a = \frac{V'_a}{2} = 10\sqrt{3} \angle -30^\circ$$

$$I_b = \frac{V'_b}{2} = 10\sqrt{3} \angle -150^\circ$$
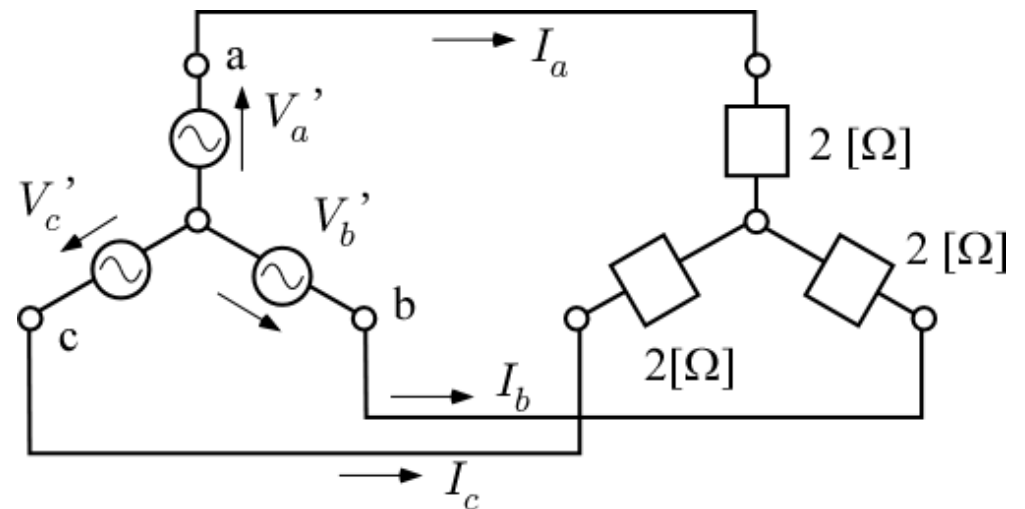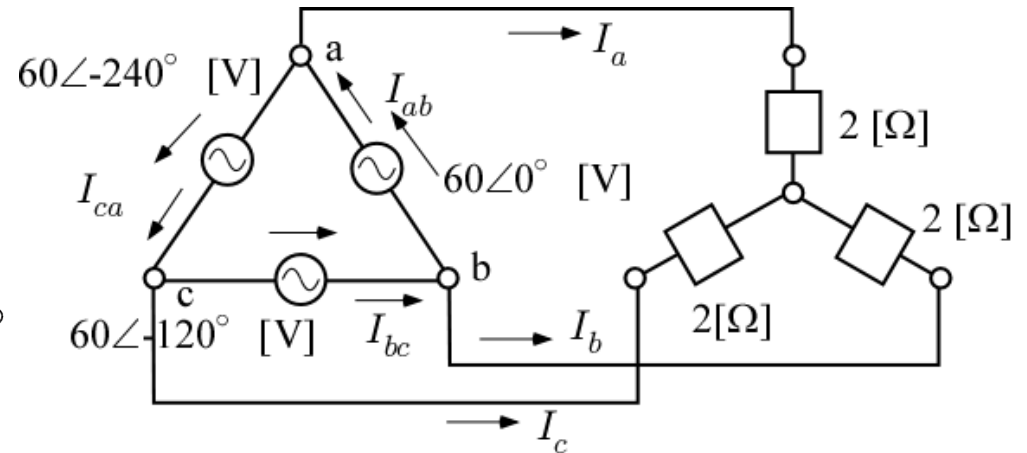
$$I_c = \frac{V'_c}{2} = 10\sqrt{3} \angle -270^\circ$$



$$I_a = I_{ab} - I_{ca}$$

$I_{ab} = I \angle 0^\circ$, $I_{ca} = I \angle -240^\circ$ と仮定

$$I_a = I - I \left(-\frac{1}{2} + j\frac{\sqrt{3}}{2} \right) = \frac{I}{2} (3 - j\sqrt{3}) = \sqrt{3}I \angle -30^\circ$$

I_a は I_{ab} より大きさが $\sqrt{3}$ 倍, 位相が 30° 遅れる



I_{ab} は I_a より大きさが $\frac{1}{\sqrt{3}}$ 倍, 位相が 30° 進む

$$I_{ab} = I_a \frac{1}{\sqrt{3}} \angle 30^\circ = 10 \angle 0^\circ$$

$$I_{bc} = I_b \frac{1}{\sqrt{3}} \angle 30^\circ = 10 \angle -120^\circ$$

$$I_{ca} = I_c \frac{1}{\sqrt{3}} \angle 30^\circ = 10 \angle -240^\circ$$

第 23 章 : 対称3相交流回路

23.2 対称3相交流回路

23.3 対称3相交流電圧のY- Δ 変換

23.5 3相負荷インピーダンスのY- Δ 変換

キーワード : Δ - Δ 結線, Y- Δ 変換, Δ -Y変換

学習目標 : 平衡 Δ - Δ 結線, Y- Δ 変換, Δ -Y変換を理解できる。